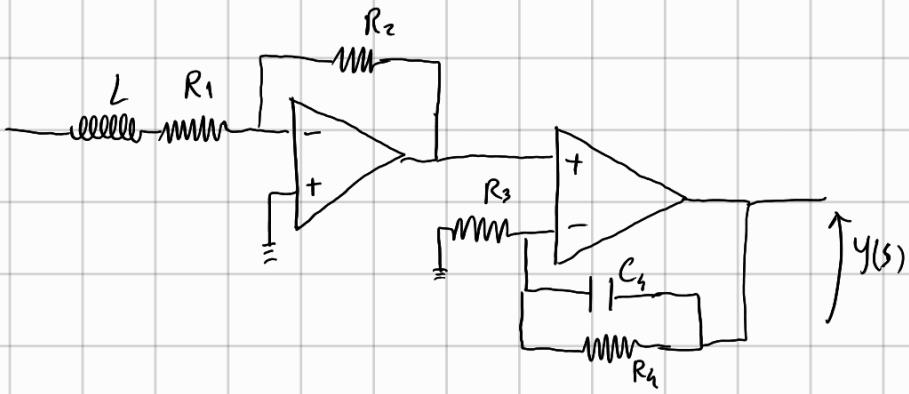


1)



$$Z_{1in}(s) = R_1 + sL$$

$$W_1(s) = -\frac{R_2}{R_1 + sL} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + s\frac{L}{R_1}}$$

$$Z_{2in}(s) \cdot R_3$$


$$Z_{2out}(s) = \frac{R_4}{1 + R_4 C_4 s}$$

$$W_2(s) = 1 + \frac{R_4}{R_3} \cdot \frac{1}{1 + R_4 C_4 s} =$$

$$= \frac{R_4 + R_3(1 + R_4 C_4 s)}{R_3(1 + R_4 C_4 s)}$$

$$W(s) = -\frac{R_2}{R_1} \cdot \left(\frac{1}{1 + s\frac{L}{R_1}} \right) \cdot \frac{R_4 + R_3(1 + R_4 C_4 s)}{R_3(1 + R_4 C_4 s)}$$

2)

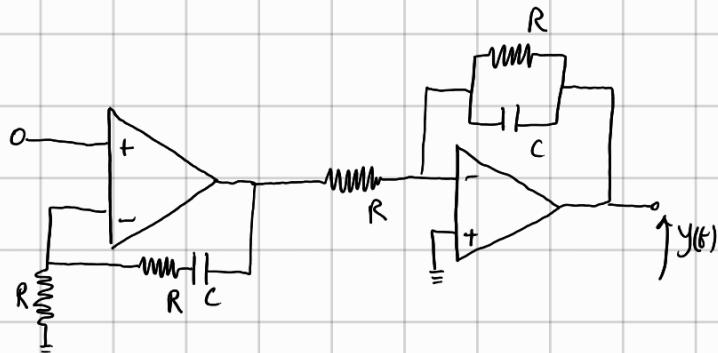

$$W_2(s) = -\frac{Z_{out}(s)}{Z_{in}(s)}$$

$$Z_{out}(s) = \frac{R}{1+RCS}$$

$$W_1(s) = 1 + \frac{Z_{out}(s)}{Z_{in}(s)}$$

$$Z_{out}(s) = R + \frac{1}{sC} = \frac{1+RCS}{sC}$$


$$W_1(s) = 1 + \frac{1+RCS}{RCS} = \frac{1+2RCS}{RCS}$$

$$W_2(s) = -\frac{1+2RCS}{(1+RCS)(RCS)}$$


$$\gamma_1 = \frac{1}{RC} \quad \gamma_2 = 0.5\gamma_1$$



LM358:

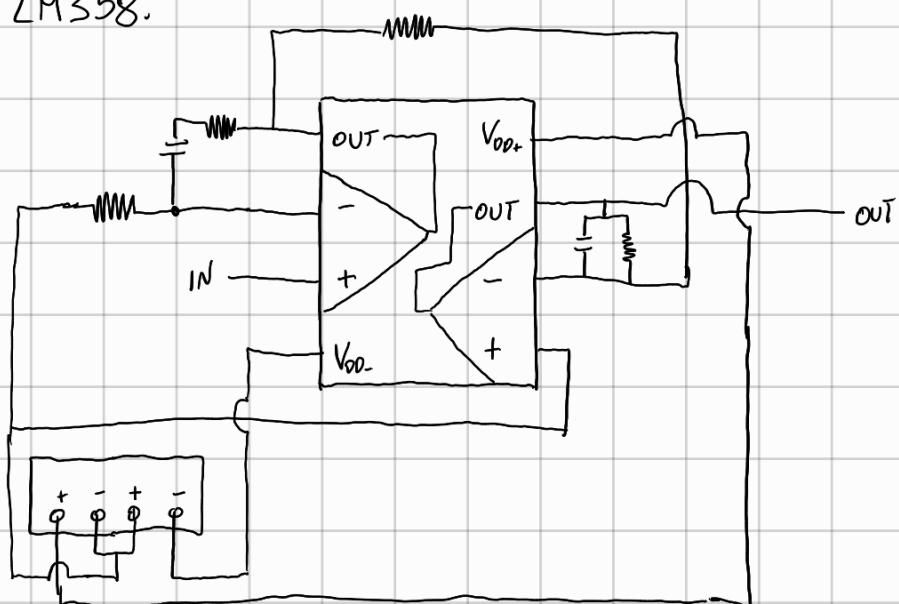

3)

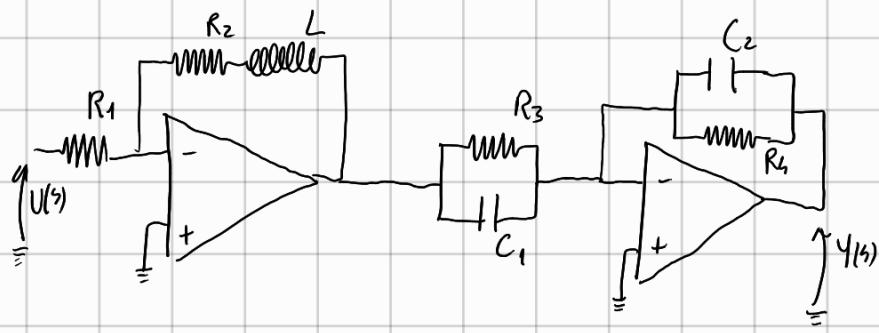

$$Z_{out1}(s) = R_2 + sL$$


$$W_1(s) = -\left(\frac{R_2 + sL}{R_1}\right) = -\frac{R_2}{R_1} \left(1 + \frac{sL}{R_2}\right)$$


$$Z_{out2}(s) = \frac{R_4}{1 + R_4 C_2 s}$$

$$Z_{in2}(s) = \frac{R_3}{1 + R_3 C_1 s}$$


$$W_2(s) = -\frac{R_4}{R_3} \cdot \frac{1 + R_3 C_1 s}{1 + R_4 C_2 s}$$
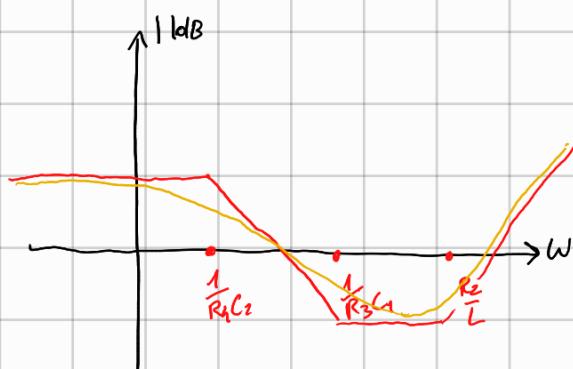
$$W(s) = \frac{R_2}{R_1} \cdot \frac{\underbrace{\left(1 + \frac{sL}{R_2}\right)}_1 \underbrace{\left(1 + R_3 C_1 s\right)}_2}_{3} \quad \text{---}$$



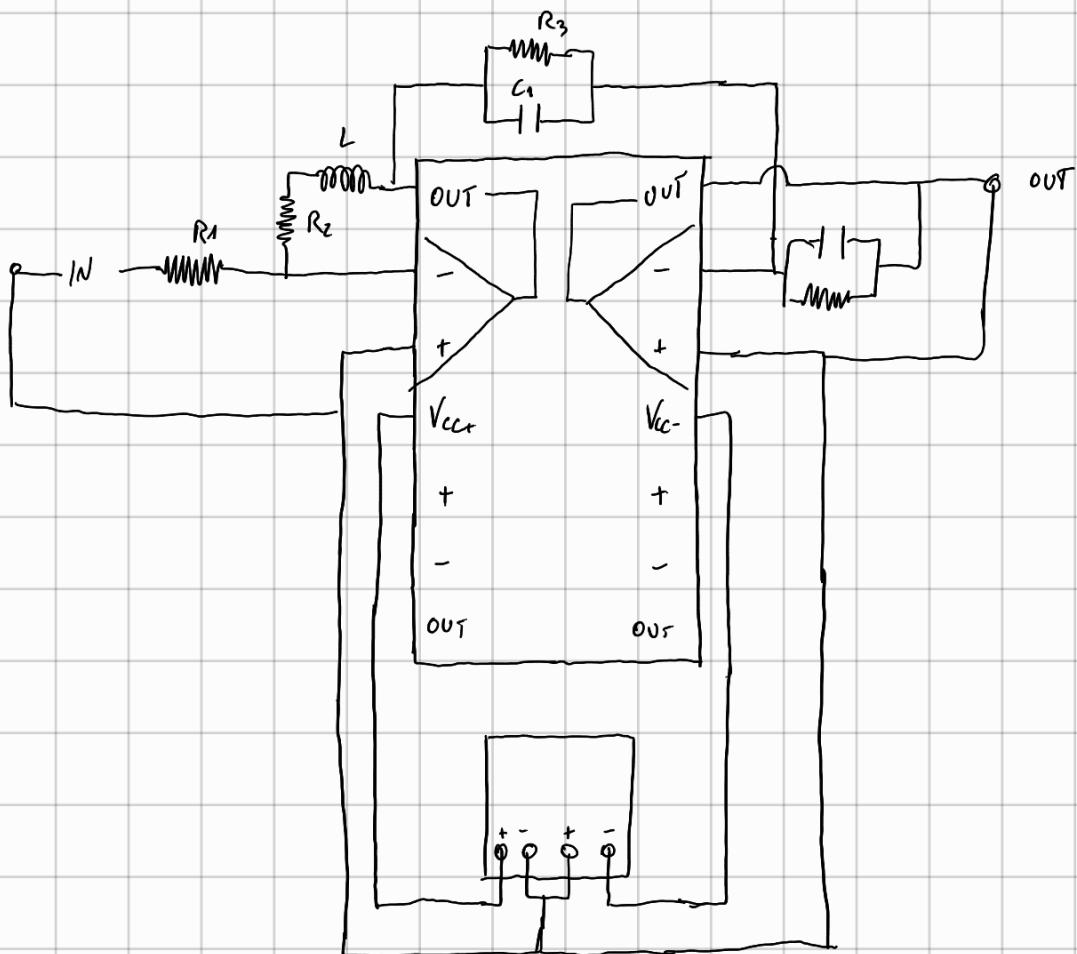

2)

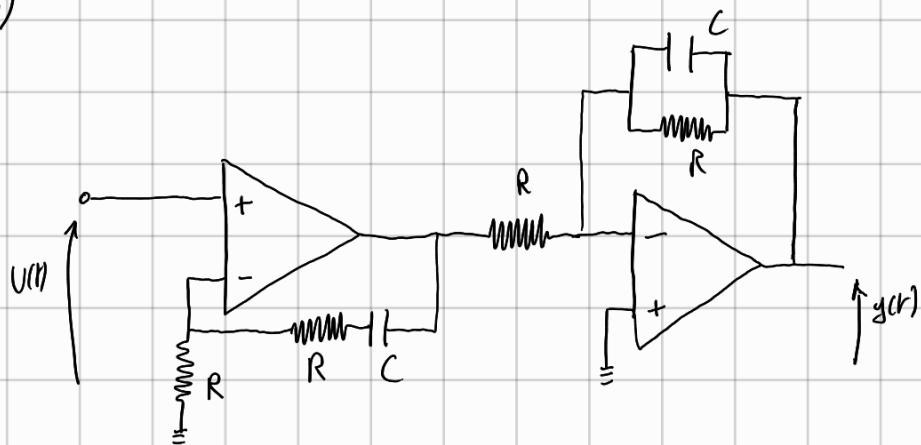




$$Z_{out,i}(s) = R + \frac{1}{sC} = \frac{1 + RCS}{sC}$$

$$W_i(s) = 1 + \frac{1 + RCS}{RCS} = \frac{1 + 2RCS}{RCS}$$

$$W_i(s) = \frac{1}{1 + RCS}$$
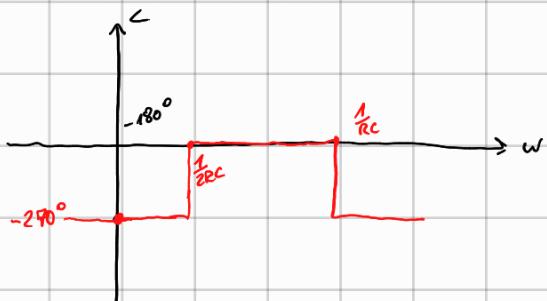
$$W(s) = -\frac{1 + 2RCS}{1 + RCS} \cdot \frac{1}{RCS}$$




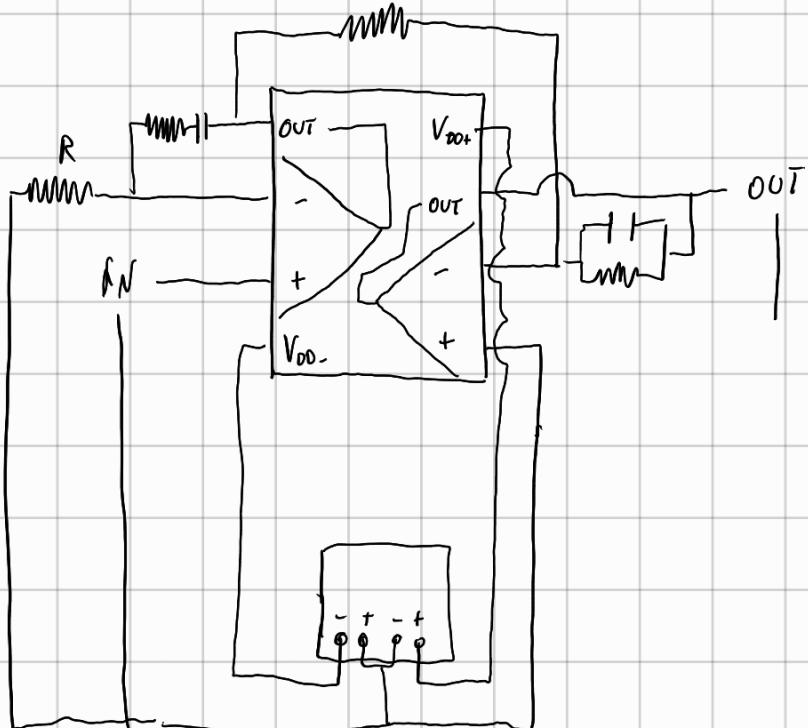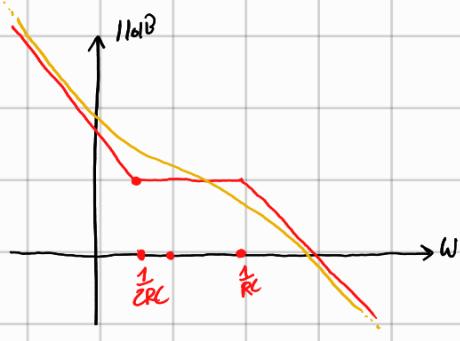

1)

$$\alpha = 2 \quad \gamma_1 = 0.7 \text{ (zero)} \quad (\text{non inverte})$$

$$\gamma_2 = 0.2 \text{ (inv)}$$

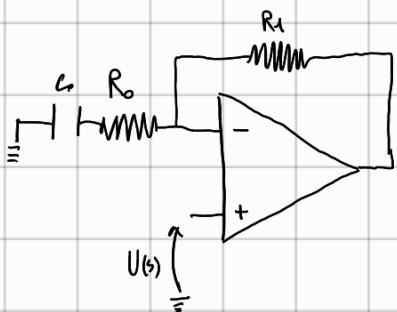

$$Z_{\text{out}} = R_1 \quad Z_{\text{in}}(s) = R_o + \frac{1}{sC_o} = \frac{1 + R_o C_o s}{sC_o} \quad W(s) = 1 + \frac{R_1 C_o s}{1 + R_o C_o s} = \frac{1 + (R_o + R_1) C_o s}{1 + R_o C_o s}$$


$$(R_o + R_1) C_o = 0.7$$

$$R_o C_o = 0.2$$



$$R_o = 100 \text{ k}\Omega$$

$$C_o = 2 \cdot 10^{-6} \text{ F} = 2 \text{ nF}$$


$$R_1 = 250 \text{ k}\Omega$$

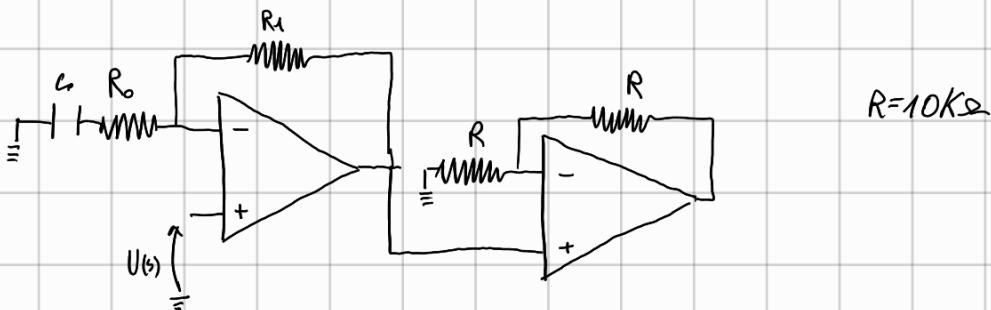
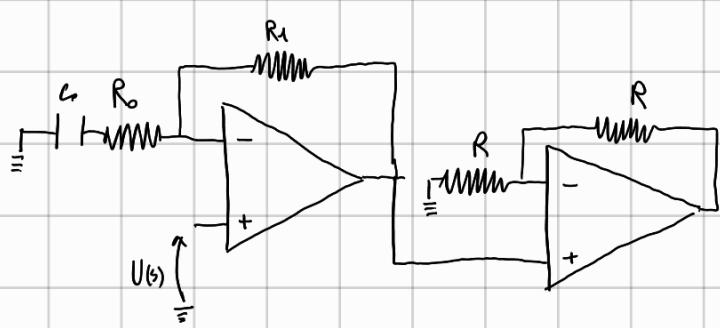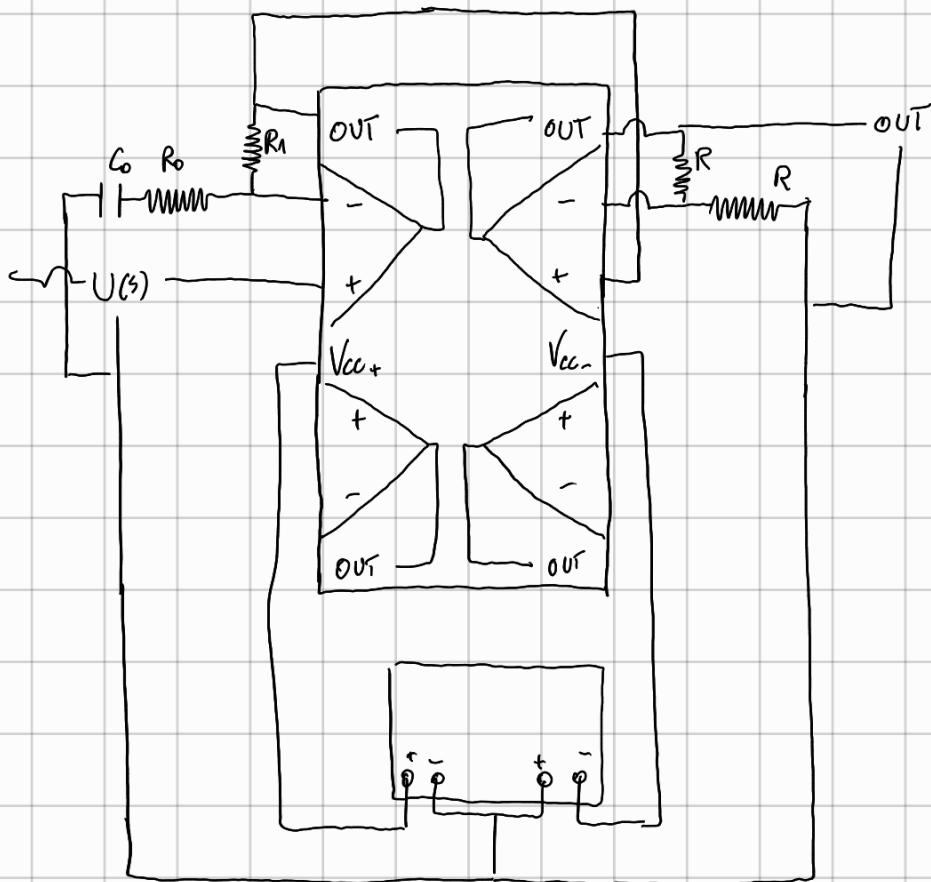
$$W(s) = \left(1 + \frac{R}{R_o}\right) \cdot \frac{1 + (R_o + R_1) C_o s}{1 + R_o C_o s}$$




4)

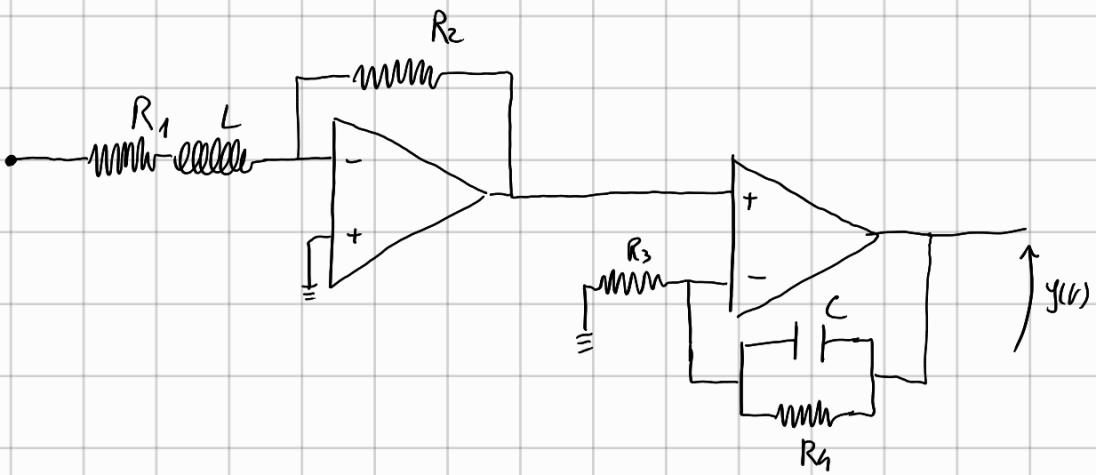


$$Z_{\text{dm}_1}(s) = R_1 + sL \quad W(s) = -\frac{R_2}{R_1 + sL} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + s \frac{L}{R_1}}$$


$$Z_{\text{out}_2}(s) = \frac{R_4}{1 + R_4 Cs} \quad Z_{\text{dm}_2}(s) = R_3 \quad W(s) = 1 + \frac{R_4}{R_3} \cdot \frac{1}{1 + R_4 Cs} = \frac{R_3(1 + R_4 Cs) + R_4}{1 + R_4 Cs}$$
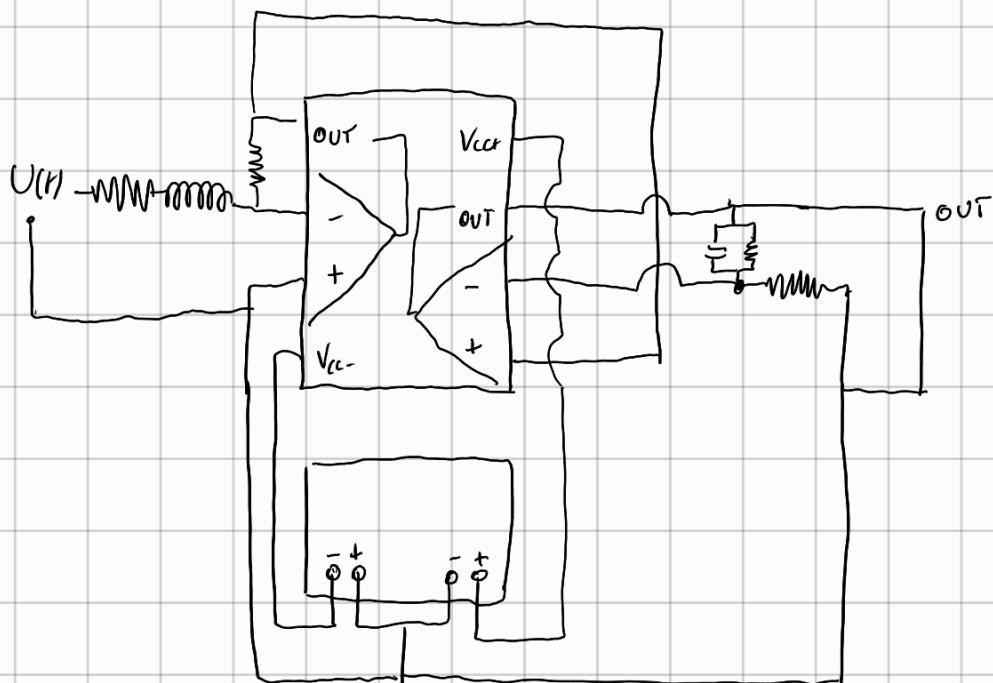
$$W(s) = -\frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{L}{R}s} \cdot \frac{(R_4 + R_3) + R_3 R_4 Cs}{1 + R_4 Cs}$$



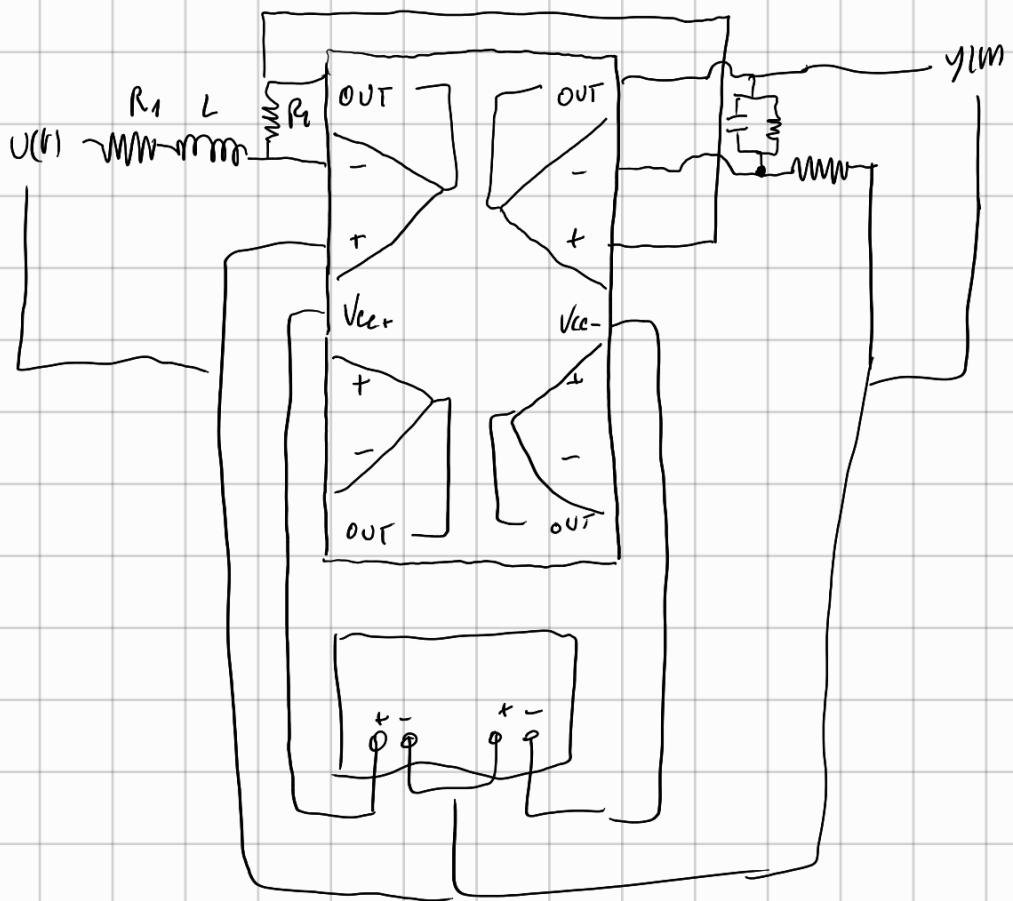

1)

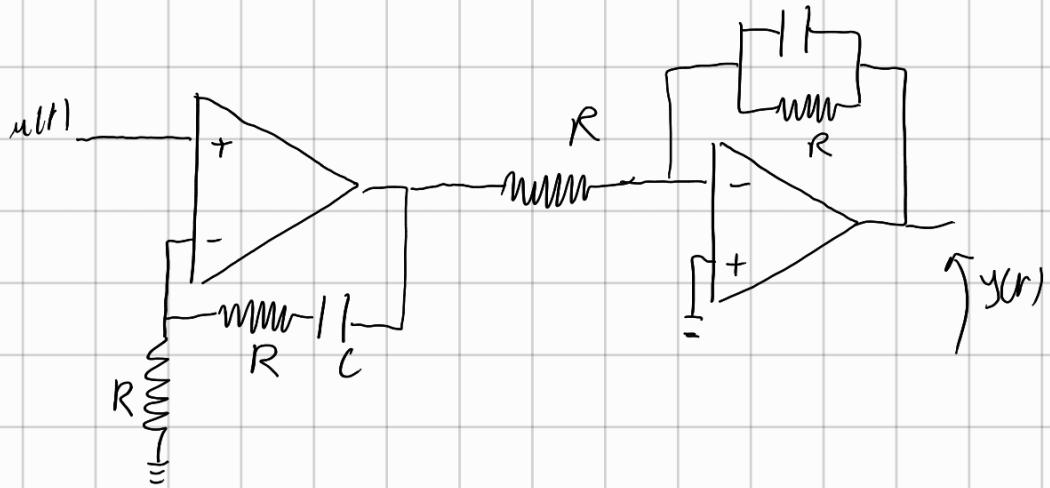

$$Z_{out1}(s) = R + \frac{1}{sC} = \frac{1 + RCS}{sC} \quad Z_{in}(s) = R$$


$$W_1(s) = 1 + \frac{Z_{out1}(s)}{Z_{in}(s)} = 1 + \frac{1 + RCS}{RCS} = \frac{1 + 2RCS}{RCS}$$

$$W_2(s) = -\frac{1}{1 + RCS}$$


$$W(s) = -\frac{1 + 2RCS}{(1 + RCS) \cdot RCS}$$

$$\varphi_1 = 2RC \text{ (zero)}$$

$$\varphi_2 = RC \text{ (pole)}$$

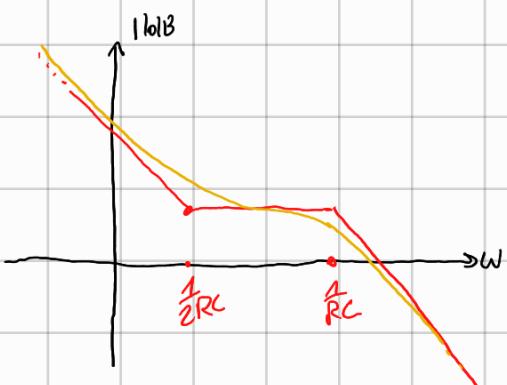


LM358:

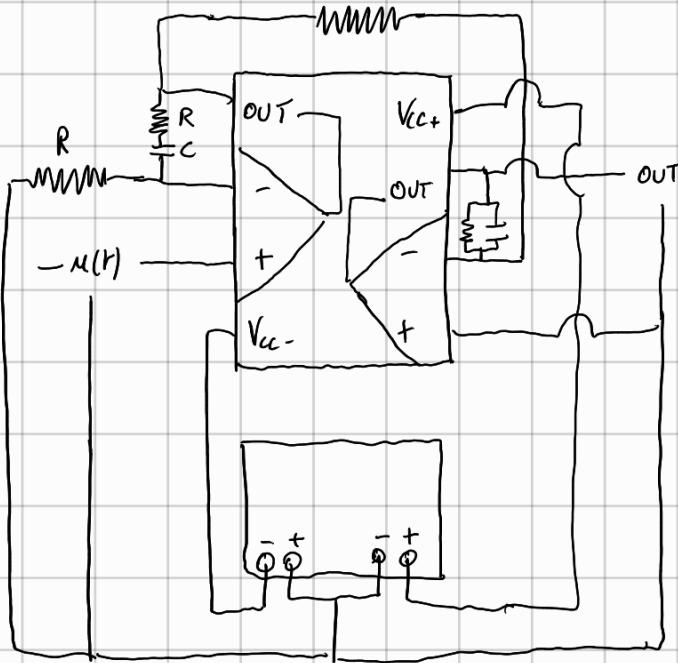

OUT	OUT'
-	-
+	+
V_{CC+}	V_{CC-}
+	+
-	-
OUT	OUT'

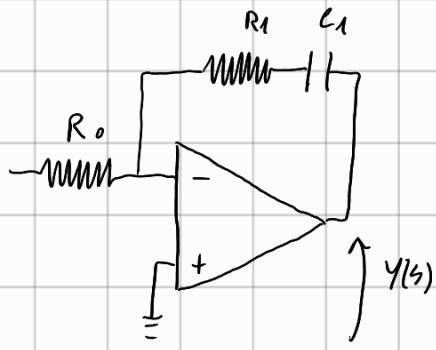4) REGOLATORE PI con K_p a 10, $T_i = 10$



$$-\left(\frac{1}{R_o C_1 s} + \frac{R_1}{R_o} \right)$$

$$Z_{out}(s) = R_1 + \frac{1}{sC_1} = \frac{1 + R_1 C_1 s}{sC_1}$$

$$W(s) = -\frac{1 + R_1 C_1 s}{R_o C_1 s} = -\frac{R_1}{R_o} \left(1 + \frac{1}{R_1 C_1 s} \right)$$


$$K = \frac{R_1}{R_o} \quad T_i = R_1 C_1$$

$$R_1 = 500 k\Omega$$


$$R_o = 50 k\Omega$$
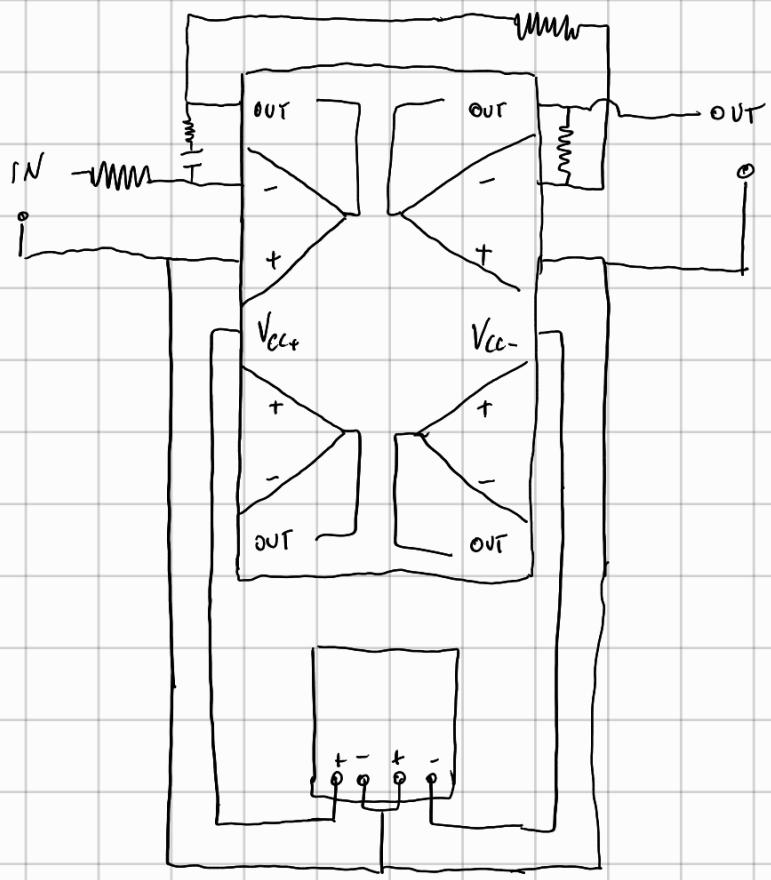
$$C_1 = \frac{10}{500 \cdot 10^3} = 20 \mu F$$





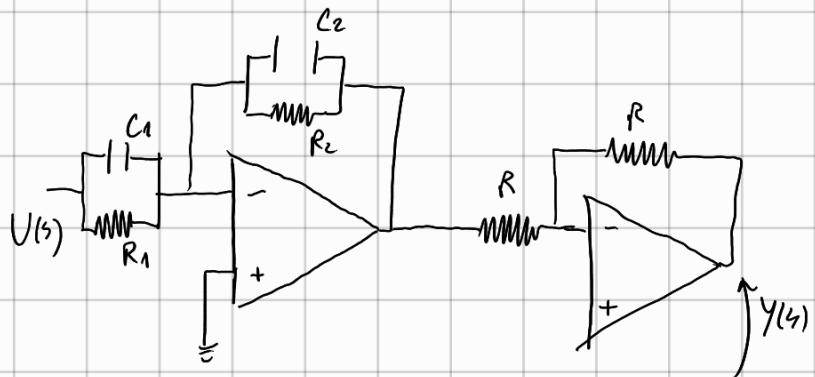RETE RITARDATRICE CON POLO CON $\varphi=0.5$, ZERO CON $\varphi=0.1$
 (GUADAGNO UNITARIO)



$$Z_{out_1}(s) = \frac{R_2}{1 + R_2 C_2 s}$$

$$Z_{out_2}(s) = \frac{R_1}{1 + R_1 C_1 s}$$


$$W(s) = \frac{R_2}{R_1} \cdot \frac{1 + R_1 C_1 s}{1 + R_2 C_2 s}$$


$$R_1 C_1 = 0.1$$

$$R_2 C_2 = 0.5$$


$$R_1 = 100 \text{ k}\Omega = R_2$$
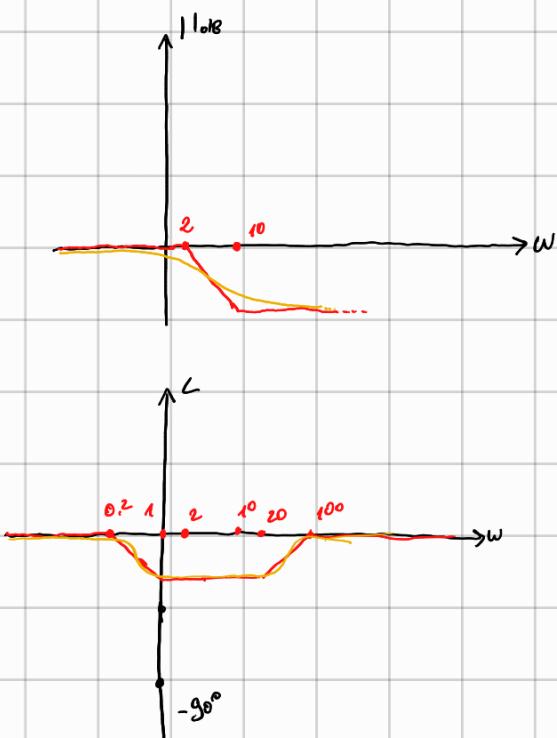
$$C_2 = 5 \text{ MF} \quad C_1 = 1 \text{ MF}$$



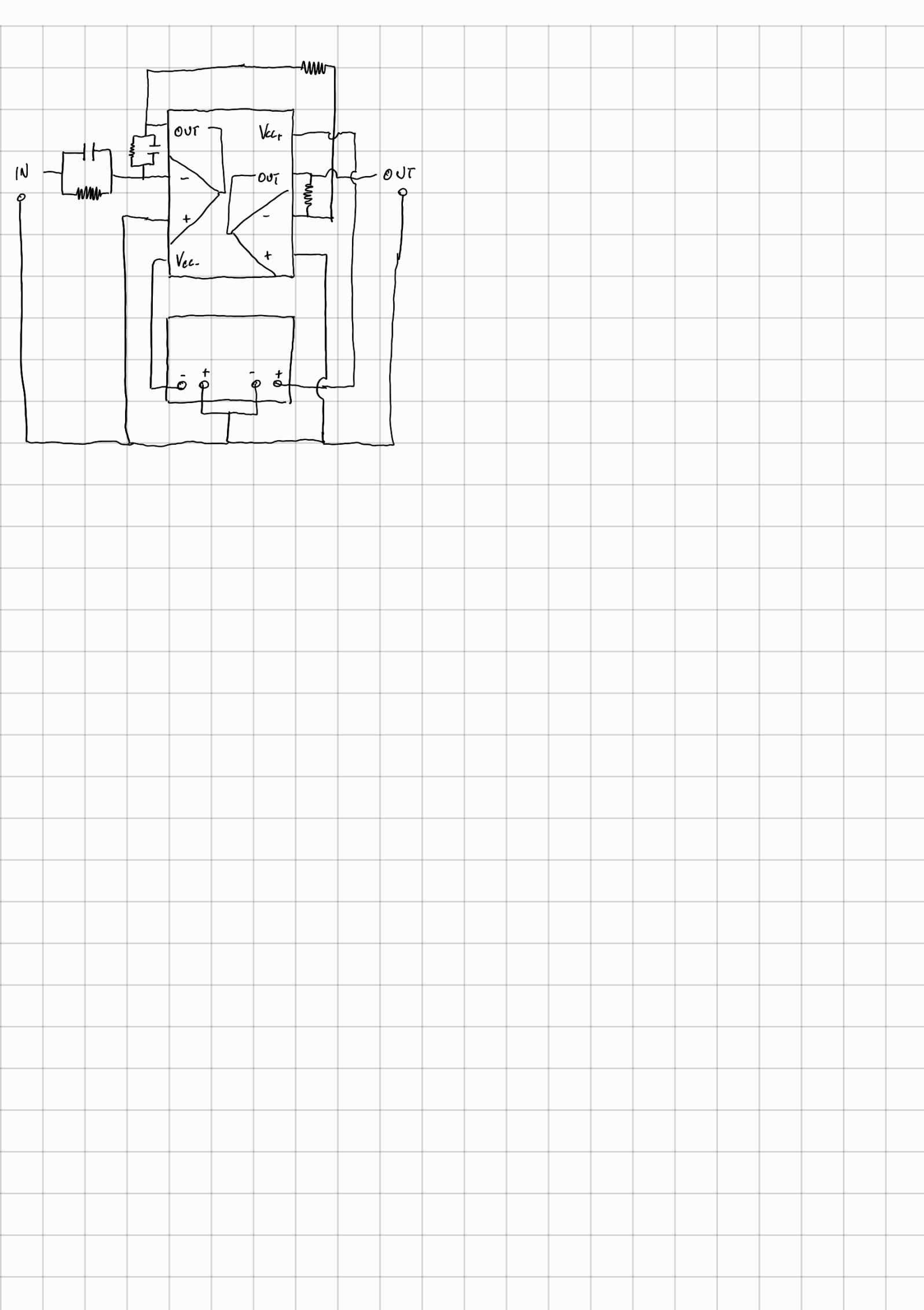

PASSA BANDA 10Hz - 100Hz

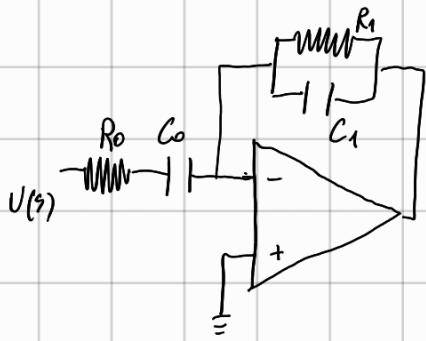


$$Z_{out}(s) = \frac{R_1}{1 + R_1 C_1 s} \quad Z_{in}(s) = R_0 + \frac{1}{Cs} = \frac{1 + R_0 C s}{Cs}$$

$$W(s) = \frac{R_1 C s}{(1 + R_1 C s)(1 + R_0 C s)}$$


$$R_0 C_0 = \frac{1}{\omega_1} \quad \frac{1}{\omega_1} = 2\pi f_0 = 62.8 \Rightarrow \frac{1}{R_0 C_0} = 6.28$$

$$R_0 = 100k\Omega \quad C_0 = 159 \text{ mF}$$
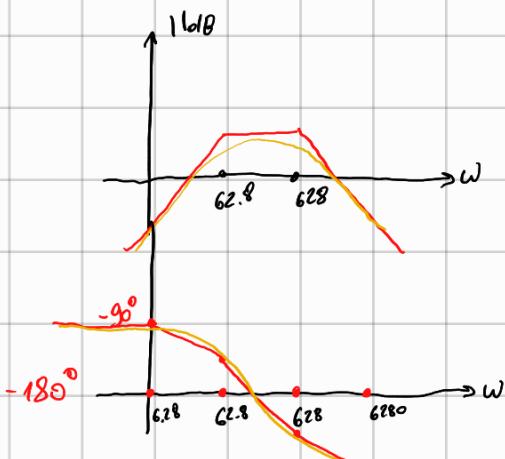
$$R_1 = 10k\Omega \quad C_1 = 159 \text{ mF}$$



3)

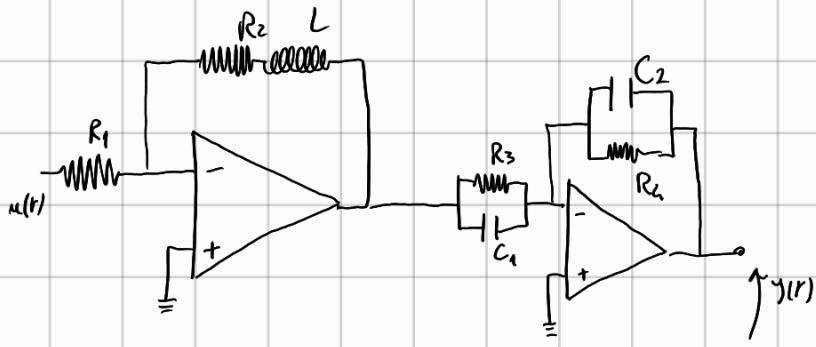

$$Z_{out1}(s) = R_2 + sL$$

$$W_1(s) = -\frac{R_2 + sL}{R_1} = -\left(\frac{R_2}{R_1} + \frac{sL}{R_1}\right)$$

$$Z_{out2}(s) = \frac{R_4}{1 + R_4 C_2 s}$$

$$Z_{in2}(s) = \frac{R_3}{1 + R_3 C_1 s}$$

$$W(s) = -\frac{R_4}{R_3} \cdot \frac{1 + \frac{L}{R_2} s}{1 + R_4 C_2 s}$$

$$W(s) = \frac{R_4}{R_1 R_3} \cdot \frac{(R_2 + sL)(1 + R_3 C_1 s)}{(1 + R_4 C_2 s)} = \frac{R_4 R_2}{R_1 R_3} \cdot \frac{\left(1 + \frac{L}{R_2} s\right)(1 + R_3 C_1 s)}{(1 + R_4 C_2 s)}$$

LM358

